

# University of Mumbai

## Examination 2020

Program: First Year Engineering

Curriculum Scheme: Rev2019 'C' Scheme


Examination: First Year Semester I

Course Code: FEC105 and Course Name: Basic Electrical Engineering

Time: 1 hour

Max. Marks: 50


For the students:- All the Questions are compulsory and carry equal marks .

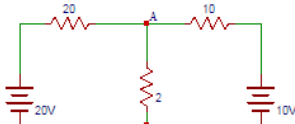Q1.	Find the voltage across $2\Omega$ resistor due to $20V$ source in the circuit shown below 
Option A:	1V
Option B:	1.5V
Option C:	2V
Option D:	2.5V
Q2.	What is the correct expression for the RMS value of current?
Option A:	$I_{rms}=I_m/2$
Option B:	$I_{rms}=I_m/\sqrt{2}$
Option C:	$I_{rms}=I_m/4$
Option D:	$I_{rms}=I_m$
Q3.	In a balanced three-phase system-delta load, if we assume the line voltage is $V_{RY} = V\angle 0^\circ$ as a reference phasor. Then the source voltage $V_{YB}$ is?
Option A:	$V\angle 0^\circ$
Option B:	$V\angle -120^\circ$
Option C:	$V\angle 120^\circ$
Option D:	$V\angle 240^\circ$
Q4.	The full-load copper loss of a transformer is 1600 W. At half-load, what will be the copper loss?
Option A:	6400 W
Option B:	1600 W
Option C:	800 W
Option D:	400 W
Q5.	Which of the following load application normally needs starting torque more than the rated torque?
Option A:	Blowers
Option B:	Conveyors
Option C:	Air compressors
Option D:	Centrifugal pumps
Q6.	Determine the equivalent Thevenin's voltage between terminals A and B in the circuit shown below

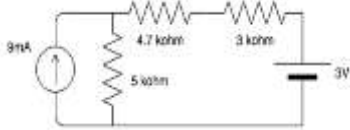
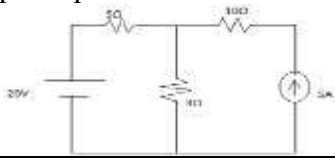
**University of Mumbai**  
**Examination 2020**

Option A:	0.333V
Option B:	3.33V
Option C:	33.3V
Option D:	333V
Q7.	If the phasors are drawn to represent the maximum values instead of the RMS values, what would happen to the phase angle between quantities?
Option A:	Increases
Option B:	Decreases
Option C:	Remains constant
Option D:	Becomes zero
Q8.	Which type of device is a stepper motor?
Option A:	Electromechanical
Option B:	Electrochemical
Option C:	Embedded system
Option D:	Electromagnetic
Q9.	In normal dc machines operating at full-load conditions, which is the most powerful electromagnet?
Option A:	Field winding
Option B:	Interpole Winding
Option C:	Interpole and compensating winding together
Option D:	Armature winding
Q10.	A three phase, balanced delta connected load of $(4+j8) \Omega$ is connected across a 400V, $3\Phi$ balanced supply. Determine the phase current $I_R$ . Assume the phase sequence to be $R_{YB}$ .
Option A:	$44.74\angle -63.4^\circ$ A
Option B:	$44.74\angle 63.4^\circ$ A
Option C:	$45.74\angle -63.4^\circ$ A
Option D:	$45.74\angle 63.4^\circ$ A
Q11.	Find the voltage drop across $6\Omega$ resistor in the circuit below, using Norton's Theorem
Option A:	6.58V
Option B:	7.58V
Option C:	8.58V
Option D:	9.58V


**University of Mumbai**  
**Examination 2020**

Q12.	A three phase induction motor is sometimes called a generalized transformer in so far as voltage and frequency transformation has been concerned. How a three phase induction motor operates when rotor frequency is equal to stator frequency?
Option A:	It will not operate
Option B:	It will operate as induction motor only
Option C:	It will operate as induction generator
Option D:	It will operate in braking mode
Q13.	If two current phasors, having magnitude 5A and 10A intersect at an angle of 60 degrees, calculate the resultant current.
Option A:	12.23A
Option B:	12.54A
Option C:	13.23A
Option D:	14.24A
Q14.	Calculate the total current in the circuit using source transformation
	
Option A:	2.3mA
Option B:	4.3mA
Option C:	3.3mA
Option D:	1.3mA
Q15.	For achieving high starting torque and high operating efficiency an induction motor should have _____ rotor circuit resistance and _____ circuit resistance under operating condition.
Option A:	High, low
Option B:	Low, high
Option C:	Low, low
Option D:	High, high
Q16.	Which of the following is the example to describe the efficiency of power transfer?
Option A:	Communication systems
Option B:	Power utility systems
Option C:	Instrumentation systems
Option D:	Telecom systems
Q17.	A resistance of $7\Omega$ is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V, 50Hz sinusoidal supply. Calculate the phase difference.
Option A:	-55.1
Option B:	55.1
Option C:	66.1
Option D:	-66.1
Q18.	If a resistor $R_x$ is connected between nodes X and Y, $R_y$ between X and Y,

**University of Mumbai**  
**Examination 2020**

	$R_z$ between Y and Z to form a delta connection, then after transformation to star, the resistor at node X is?
Option A:	$R_x R_y / (R_x + R_y + R_z)$
Option B:	$R_x R_z / (R_x + R_y + R_z)$
Option C:	$R_z R_y / (R_x + R_y + R_z)$
Option D:	$(R_x + R_y) / (R_x + R_y + R_z)$
Q19.	Find the equivalent resistance between node 1 and node 3 in the star connected circuit shown below 
Option A:	30Ω
Option B:	31Ω
Option C:	32Ω
Option D:	33Ω
Q20.	A single phase transformer has specifications as 250 KVA, 11000V/415V, 50 Hz. What are the values of primary and secondary currents?
Option A:	Primary current = 602.4A, Secondary current = 22.7A
Option B:	Secondary current = 202.7A, Primary current = 602.4A
Option C:	Primary current = 22.7A, Secondary current = 602.4A
Option D:	Primary current = 11.35A, Secondary current = 301.2A
Q21.	Find the current in the 3Ω resistor of the given network using Superposition principle. 
Option A:	2.5A
Option B:	3.125A
Option C:	6.525A
Option D:	5.625A
Q22.	For a transformer given of 100 kVA, 220V/6000V transformer, short circuit test is performed. What current rating is needed?
Option A:	30A
Option B:	445A
Option C:	60A
Option D:	55A
Q23.	The three impedances $Z_1 = 20\angle 30^\circ \Omega$ , $Z_2 = 40\angle 60^\circ \Omega$ , $Z_3 = 10\angle -90^\circ \Omega$ are delta-connected to a 400V, 3Φ system. Determine the phase current $I_Y$
Option A:	(10-j0) A
Option B:	(10+j0) A
Option C:	(-10+j0) A
Option D:	(-10-j0) A

**University of Mumbai**  
**Examination 2020**

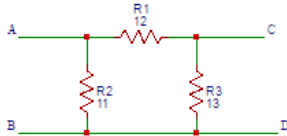Q24.	Find the equivalent resistance at node A in the delta connected circuit shown in the figure below. 
Option A:	1Ω
Option B:	2Ω
Option C:	3Ω
Option D:	4Ω
Q25.	The input power to a three-phase load is 10kW at 0.8 Pf. Two watt meters are connected to measure the power. Find the reading of higher reading wattmeter.
Option A:	7.165
Option B:	6.165
Option C:	6.165
Option D:	4.165