

University of Mumbai

Examination 2020

Program: Electronics & Telecommunication Engineering

Curriculum Scheme: Rev2016



Examination: Third Year Semester III

Course Code: _ECC304_____ and Course Name: Circuit Theory and Networks

Time: 1 hour

Max. Marks: 50

Note to the students:- All the Questions are compulsory and carry equal marks .

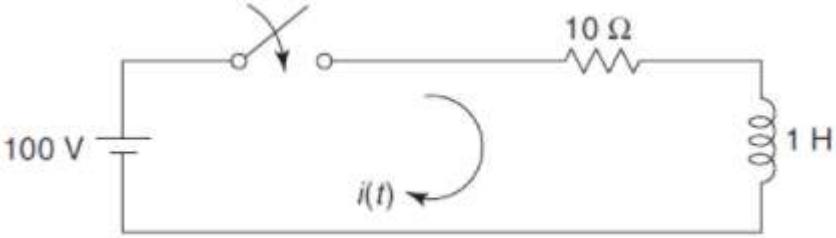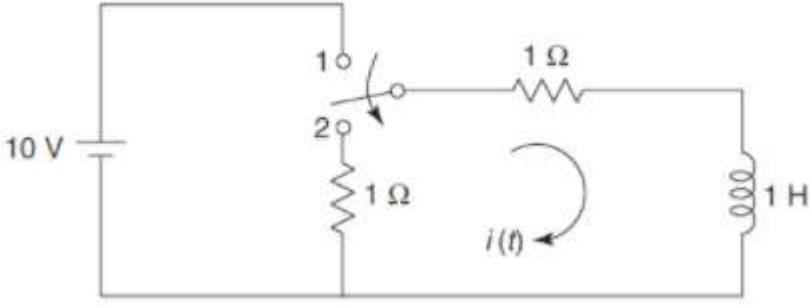Q1.	The network having admittance function $Y(s)=(4s^2+6s)/(s+1)$
Option A:	RC function
Option B:	LC function
Option C:	RLC function
Option D:	None of the above
Q2.	In the given network, the switch is closed at $t = 0$. With zero current in the inductor, find i at $t=0^+$
	
Option A:	0 A
Option B:	1 A
Option C:	2 A
Option D:	3 A
Q3.	In the network, the switch is moved from position 1 to position 2 at $t=0$, steady state condition having been established in the position 1. Determine $i(t)$ for $t>0$.
	
Option A:	$10e^{-(-2t)} A$
Option B:	$10e^{(2t)} A$
Option C:	$20e^{-(-2t)} A$
Option D:	$20e^{(2t)} A$
Q4.	In the network, the switch is moved from a to b at $t=0$. Determine $i(t)$

University of Mumbai
Examination 2020


Option A:	$10e^{-(-0.5t)} A$
Option B:	$10e^{(-0.5)} A$
Option C:	$10e^{(0.5t)} A$
Option D:	$10e^{(0.5)} A$
Q5.	The switch is opened at time $t=0$. Determine $v(t)$ for $t>0$.
Option A:	$4t^*e^{(-2t)} A$
Option B:	$4t^*e^{(2t)} A$
Option C:	$2t^*e^{(-2t)} A$
Option D:	$4t^*e^{(-2t)} V$
Q6.	Determine the driving point impedance of the network shown in figure
Option A:	$8s^3 + 4s$
Option B:	$16s^4 + 12s^2 + 1$
Option C:	$\frac{16s^4 + 12s^2 + 1}{8s^3 + 4s}$

University of Mumbai
Examination 2020

Option D:	None of the above
Q7.	What is the value of V_1 in the network given here?
Option A:	$5I_1$
Option B:	$-5I_1$
Option C:	$2I_2$
Option D:	$-2I_2$
Q8.	Find the current I_1 in the network shown
Option A:	1.364 A
Option B:	2.878 A
Option C:	-1.364 A
Option D:	-2.878 A
Q9.	Find the current I_2 in the network shown
Option A:	1.364 A
Option B:	2.878 A
Option C:	-1.364 A
Option D:	-2.878 A

University of Mumbai
Examination 2020

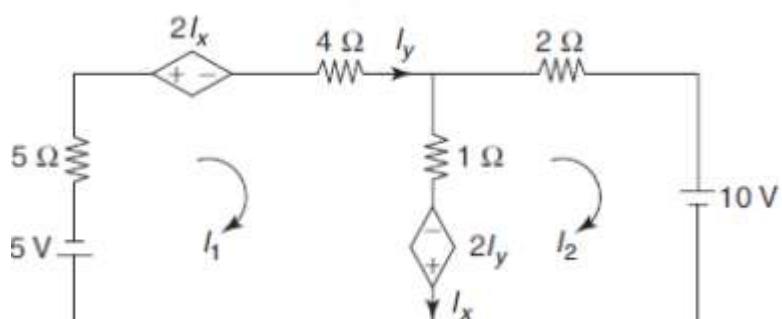Q10. Find the current I_x in the network shown




Option A: -1.514 A

Option B: 2.878 A

Option C: -2.878 A

Option D: 1.514 A

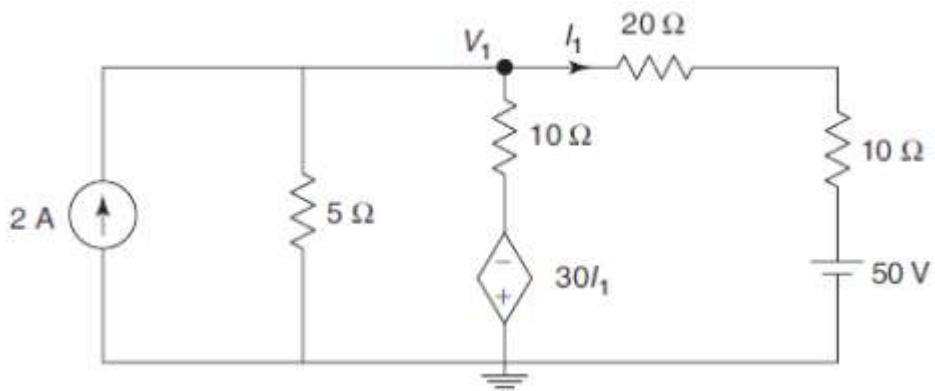Q11. Find the voltage across 5 ohms resistor in the network shown




Option A: 20 V

Option B: -20 V

Option C: 40 V

Option D: -40 V

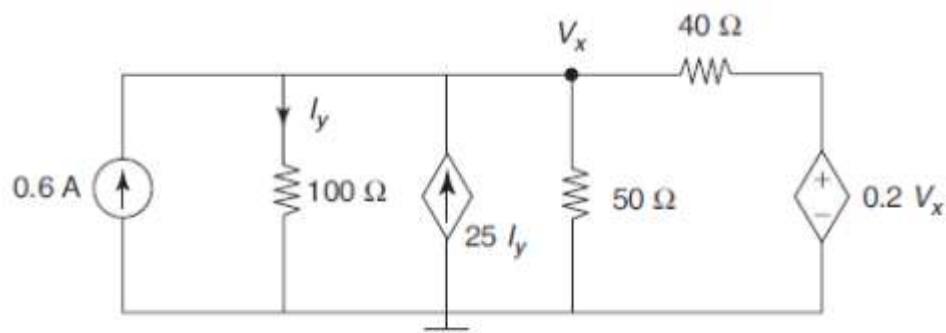Q12. Find the voltage V_x in the network given






Option A: -3 A

Option B: -3 V




Option C: -3 ohms

Option D: -3 S


University of Mumbai
Examination 2020

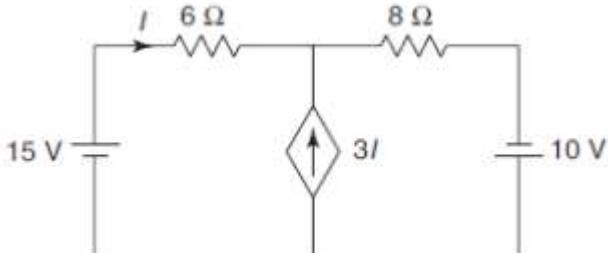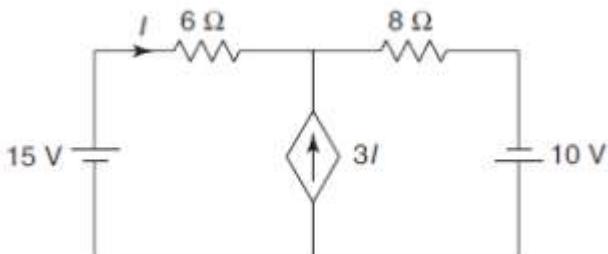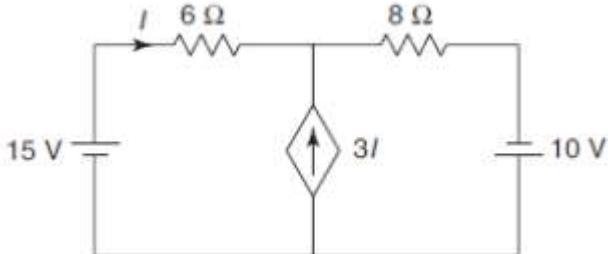Q13.	<p>When using Superposition theorem in the network given here, what will be the current through 6 ohms when only 15 V source is acting? (assuming current is in clockwise direction)</p> 
Option A:	0.3 A
Option B:	0.34 A
Option C:	0.39 A
Option D:	None of the above
Q14.	<p>When using Superposition theorem in the network given here, what will be the current through 6 ohms when only 10 V source is acting? (assuming current is in clockwise direction)</p> 
Option A:	0.2 A
Option B:	0.26 A
Option C:	0.29 A
Option D:	None of the above
Q15.	<p>When using Superposition theorem in the network given here, what will be the current through 6 ohms? (assuming current is in clockwise direction)</p> 
Option A:	1 A
Option B:	0.74 A
Option C:	0.65 A
Option D:	None of the above

University of Mumbai
Examination 2020

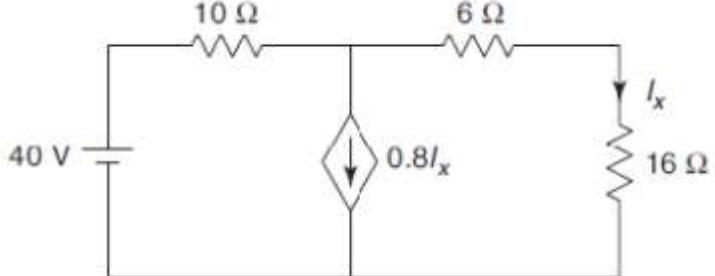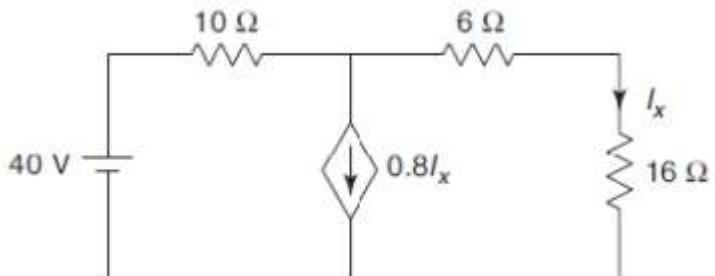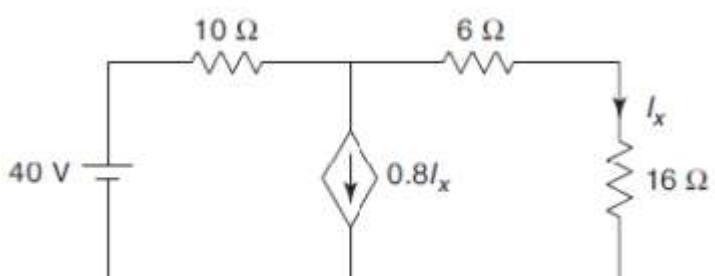Q16.	If the load resistor is 16 ohms, what is the Thevenin's equivalent voltage?
	
Option A:	10 V
Option B:	20 V
Option C:	30 V
Option D:	None of these
Q17.	If the load resistor is 16 ohms, what is the Thevenin's equivalent resistance?
	
Option A:	6 ohms
Option B:	12 ohms
Option C:	18 ohms
Option D:	24 ohms
Q18.	Determine the current in the 16 ohms resistor for the network given?
	
Option A:	0.2 A
Option B:	1 A
Option C:	2 A
Option D:	-2 A
Q19.	When the voltages and currents are to be found out from a given network, this is called as
Option A:	Network Synthesis
Option B:	Network Analysis

University of Mumbai
Examination 2020

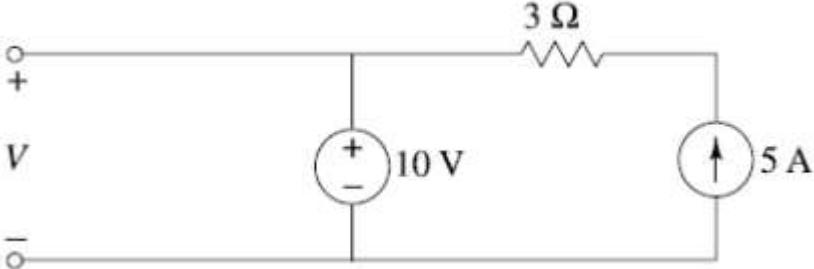Option C:	Both of the above
Option D:	None of the above
Q20.	In maximum power transfer theorem,
Option A:	$R_{TH} = RL$
Option B:	$V_{TH} = VL$
Option C:	$I_{TH} = IL$
Option D:	None of the above
Q21.	The voltage V in the figure is equal to
	
Option A:	10 V
Option B:	15 V
Option C:	5 V
Option D:	None of these
Q22.	Laplace transform changes the _____ domain function to the _____ domain function.
Option A:	time, time
Option B:	time, frequency
Option C:	frequency, time
Option D:	frequency, frequency
Q23.	The resistance element _____ while going from the time domain to frequency domain.
Option A:	does not change
Option B:	increases
Option C:	decreases
Option D:	increases exponentially
Q24.	The current in the R-L circuit at a time $t = 0+$ is?
Option A:	V/R
Option B:	R/V
Option C:	V
Option D:	R
Q25.	Find Z_{11} for the following network

**University of Mumbai
Examination 2020**

	<p>The diagram shows a circuit with four resistors and two voltage sources. A vertical line at the bottom represents the common ground reference. On the left, there is a voltage source V_1 with its positive terminal at the top. Above it, a $1\ \Omega$ resistor is connected in series with the circuit. To the right of the $1\ \Omega$ resistor, another $1\ \Omega$ resistor is connected in series. After this, a $2\ \Omega$ resistor branches off downwards to the ground. From the junction of the $1\ \Omega$ and $2\ \Omega$ resistors, a $2\ \Omega$ resistor continues upwards. Finally, a $1\ \Omega$ resistor is connected from the top of the $2\ \Omega$ resistor back to the common ground line. Currents I_1 and I_2 are indicated: I_1 flows through the first $1\ \Omega$ resistor from left to right, and I_2 flows through the last $1\ \Omega$ resistor from right to left.</p>
Option A:	11/5
Option B:	4/5
Option C:	-4/5
Option D:	6/5