

University of Mumbai
Examination 2020

Program: Electronics and Telecommunication Engineering

Curriculum Scheme: Rev2012

Examination: Third Year Semester VI

Course Code: ETC606 and Course Name: VLSI Design

Time: 1 hour

Max. Marks: 50

For the students:- All the Questions are compulsory and carry equal marks .

Q1.	The scaling factor similar to scaling factor of power speed product is:
Option A:	Power dissipation per unit area
Option B:	Switching Energy
Option C:	Power dissipation per gate
Option D:	Power dissipation of the device
Q2.	Increasing fan-out _____ the propagation delay.
Option A:	increases
Option B:	decreases
Option C:	does not affect
Option D:	exponentially decreases
Q3.	Which of the following capacitor can store more data in DRAM?
Option A:	planar capacitor
Option B:	trench capacitor
Option C:	stacked-cell
Option D:	non-polar capacitor
Q4.	The final addition sum of the numbers, 0110 & 0110 is _____
Option A:	1101
Option B:	1111
Option C:	1001
Option D:	1010
Q5.	In consistency/ justification, tracking is done
Option A:	forward from gate input to primary input
Option B:	backwards from gate input to primary output
Option C:	backwards from gate input to primary input
Option D:	forward from gate output to primary output
Q6.	To propagate the fault along the selected path to primary output, setting _____ is done.
Option A:	AND to 1
Option B:	OR to 1
Option C:	NOR to 1
Option D:	NAND to 0
Q7.	A _____ gate is used to detect the occurrence of an overflow.
Option A:	NAND

University of Mumbai
Examination 2020

Option B:	XOR
Option C:	XNOR
Option D:	AND
Q8.	What is the size of a trench capacitor in DRAM?
Option A:	1 Mb
Option B:	4-256 Mb
Option C:	8-128 Mb
Option D:	64-128 Mb
Q9.	What is the input resistance of CMOS inverter?
Option A:	high
Option B:	low
Option C:	very low
Option D:	Cannot be determined
Q10.	The static component of power dissipation is given by:
Option A:	$P = I^2.R_d$
Option B:	$P = V_{dd}^2/R_{on}$
Option C:	$P = E_g.f_o$
Option D:	$P = E_g.R_d$
Q11.	The gate delay is proportional to:
Option A:	$R_{on}.C_g$
Option B:	$R_s.C_d$
Option C:	$R_d.C_g$
Option D:	$R_{on}.C_{ox}$
Q12.	In CMOS domino logic _____ is possible.
Option A:	inverting structure
Option B:	non inverting structure
Option C:	inverting and non inverting structure
Option D:	very complex design
Q13.	How many MOSFETs are required for SRAM?
Option A:	2
Option B:	4
Option C:	6
Option D:	8
Q14.	Which method is suitable for larger operands?
Option A:	Baugh-Wooley algorithm
Option B:	Wallace trees
Option C:	Dadda multipliers
Option D:	Modified booth encoding
Q15.	Oxide breakdown occurs due to
Option A:	electrostatic charge

University of Mumbai
Examination 2020

Option B:	threshold voltage
Option C:	voltage shift
Option D:	poor input/output pad circuitry
Q16.	Exhaustive testing is suitable when N is
Option A:	small
Option B:	large
Option C:	any value for N
Option D:	very large
Q17.	In full adders the sum circuit is implemented using _____
Option A:	AND & OR gates
Option B:	NAND gate
Option C:	XOR
Option D:	XNOR
Q18.	Which is the storage element in DRAM?
Option A:	inductor
Option B:	capacitor
Option C:	resistor
Option D:	MOSFET
Q19.	In CMOS inverter, transistor is a switch having _____
Option A:	infinite on resistance
Option B:	finite off resistance
Option C:	buffer
Option D:	infinite off resistance
Q20.	The dynamic component of power dissipation is given by:
Option A:	$P = I^2 \cdot R_d$
Option B:	$P = V_{dd}^2 / R_d$
Option C:	$P = E_g \cdot f_o$
Option D:	$P = E_g \cdot R_d$
Q21.	The power dissipation per gate is scaled as:
Option A:	1
Option B:	$1 / \beta \cdot \alpha^2$
Option C:	α^2 / β
Option D:	$1 / \beta^2$
Q22.	CMOS inverter has _____ regions of operation.
Option A:	three
Option B:	four
Option C:	two
Option D:	five
Q23.	Which memory storage is widely used in PCs and Embedded Systems?
Option A:	SRAM

University of Mumbai
Examination 2020

Option B:	DRAM
Option C:	Flash memory
Option D:	EEPROM
Q24.	Internally, a computer's binary data are always transmitted on parallel channels which is commonly referred to as the _____
Option A:	Parallel bus
Option B:	Serial bus
Option C:	Data bus
Option D:	Memory bus
Q25.	Which model is used for pc board testing?
Option A:	stuck at
Option B:	stuck in
Option C:	stuck on
Option D:	stuck through